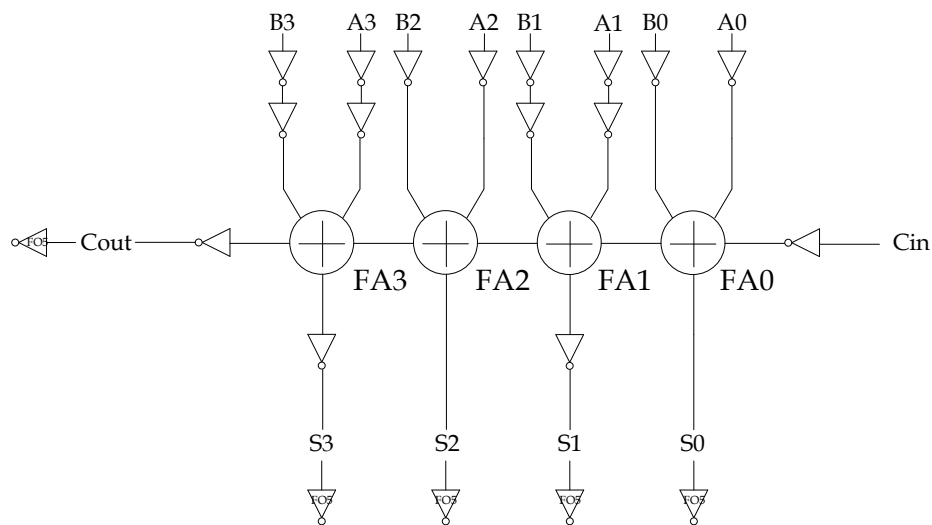



A 4-bit ripple carry adder shown in Fig. 1 is designed with fully complementary static logic gate of full adder (FA). Input signals are $A[3:0]$, $B[3:0]$, and C_{in} . Outputs are $SUM[3:0]$ and C_{out} .

(1) Try to design the fastest adder when each input signal is driven by one unit size inverter. For the output loads, 5 unit size inverters are used for each output signal. First, show your block diagrams in terms of the 1-bit FA. Second, show the circuit schematic of the FA. Use logic effort concepts (do not have to write down the procedure) to design transistor widths. Describe your design concept. (40%)

(a) The block diagram in terms of 1-bit FA:



(b) The circuit schematic of my FA:

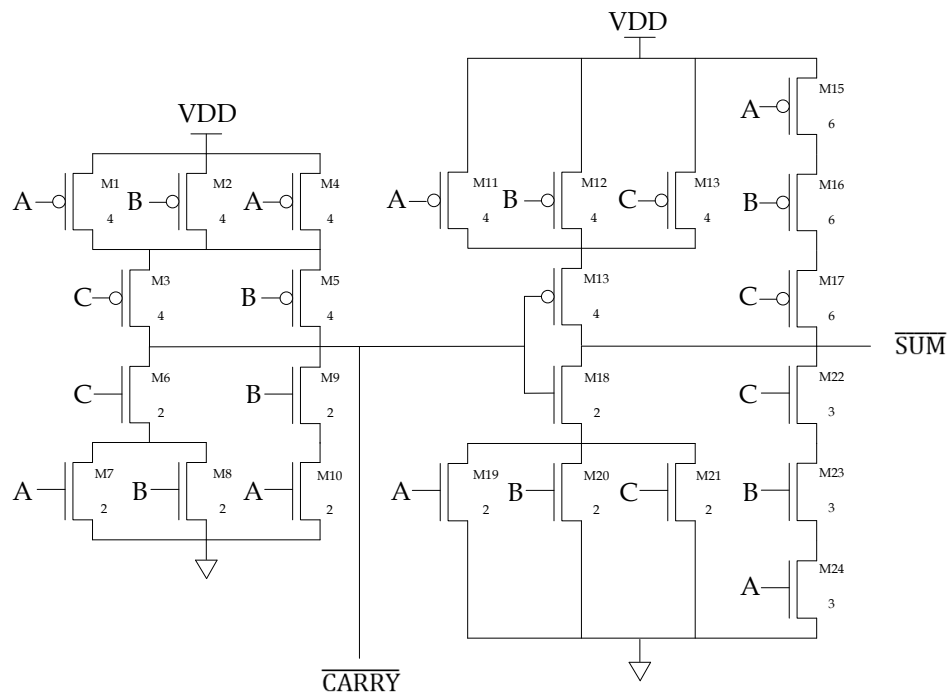

我把每個 mos 的 n_{fin} 都標在上面了。

(c) Design concept:

- 利用 FA 的 inversion property 省去 FA 與 FA 之間的 inverter 以減少 critical path 上的 delay。
- 晚到的訊號 (即 C) 要放靠近輸出的地方，可以減少 delay。
- 並聯的部分要放靠近 VDD 與 GND，以減少寄生電容對 output 訊號的影響。
- 我設定 PMOS 和 NMOS 的 size 比例為 2:1。
- RCA 的 critical path 就是由每個 FA 的 carry out 串接起來再加上 FA3 的 sum。
- FA 左半部用來產生 carry out 的 mos 要調大，這樣才推得動下一個 FA。
- FA 右半部用來產生 sum 的 mos 要調小，讓 carry out 的 loading 小一點。
- RCA 最尾端的 carry out 後面又接了 FO5。也就是說整個 critical path 的 effort delay 是 5。
- 所以我 size 的設計如下:
 - FA0 設為 unit size 的 1 倍。
 - FA1 設為 unit size 的 2 倍。
 - FA2 設為 unit size 的 3 倍。
 - FA3 設為 unit size 的 4 倍。
 - 以 FA3 為例，下圖是 FA3 的 code:

```
.subckt FA3 A B C carry_bar sum_bar
* begin of carry
M1 n1 n2 A vdd! vdd! pmos_rvt nfin = '4 * 4'
M2 n1 n3 B vdd! vdd! pmos_rvt nfin = '4 * 4'
M3 carry_bar n4 C n1 vdd! pmos_rvt nfin = '4 * 4'
M4 n2 n5 A vdd! vdd! pmos_rvt nfin = '4 * 4'
M5 carry_bar n6 B n2 vdd! pmos_rvt nfin = '4 * 4'
M6 carry_bar n7 C n3 gnd! nmos_rvt nfin = '2 * 4'
M7 n3 n8 A gnd! gnd! nmos_rvt nfin = '2 * 4'
M8 n3 n9 B gnd! gnd! nmos_rvt nfin = '2 * 4'
M9 carry_bar n10 B n4 gnd! nmos_rvt nfin = '2 * 4'
M10 n4 n11 A gnd! gnd! nmos_rvt nfin = '2 * 4'
* end of carry
* begin of sum
M11 n5 n12 A vdd! vdd! pmos_rvt nfin = 4
M12 n5 n13 B vdd! vdd! pmos_rvt nfin = 4
M13 n5 n14 C vdd! vdd! pmos_rvt nfin = 4
M14 sum_bar carry_bar n15 vdd! pmos_rvt nfin = 4
M15 n6 n16 A vdd! vdd! pmos_rvt nfin = 6
M16 n7 n17 B n6 vdd! pmos_rvt nfin = 6
M17 sum_bar n18 C n7 vdd! pmos_rvt nfin = 6
M18 sum_bar carry_bar n19 gnd! nmos_rvt nfin = 2
M19 n8 n20 A gnd! gnd! nmos_rvt nfin = 2
M20 n8 n21 B gnd! gnd! nmos_rvt nfin = 2
M21 n8 n22 C gnd! gnd! nmos_rvt nfin = 2
M22 sum_bar n23 C n9 gnd! nmos_rvt nfin = 3
M23 n9 n24 B n10 gnd! nmos_rvt nfin = 3
M24 n10 n25 A gnd! gnd! nmos_rvt nfin = 3
* end of sum
.ends
```

- 然後 FA3 去推 FO5 (5 倍的 unit size inverter)
- 這樣做的好處是我每一級負責的推力較為平均。

(d) Size for each mos:

Unit size inverter

MOS Type	size
PMOS	2
NMOS	1

FA0:

Index of MOS	size
M1	$4 \times 1 = 4$
M2	$4 \times 1 = 4$
M3	$4 \times 1 = 4$
M4	$4 \times 1 = 4$
M5	$4 \times 1 = 4$
M6	$2 \times 1 = 2$
M7	$2 \times 1 = 2$
M8	$2 \times 1 = 2$
M9	$2 \times 1 = 2$
M10	$2 \times 1 = 2$
M11	4
M12	4
M13	4
M14	4
M15	6
M16	6
M17	6
M18	2
M19	2
M20	2
M21	2
M22	3
M23	3
M24	3

FA1:

Index of MOS	size
M1	$4 \times 2 = 8$
M2	$4 \times 2 = 8$
M3	$4 \times 2 = 8$
M4	$4 \times 2 = 8$
M5	$4 \times 2 = 8$
M6	$2 \times 2 = 4$
M7	$2 \times 2 = 4$
M8	$2 \times 2 = 4$
M9	$2 \times 2 = 4$
M10	$2 \times 2 = 4$
M11	4
M12	4
M13	4
M14	4
M15	6
M16	6
M17	6
M18	2
M19	2
M20	2
M21	2
M22	3
M23	3
M24	3

FA2:


Index of MOS	size
M1	$4 \times 3 = 12$
M2	$4 \times 3 = 12$
M3	$4 \times 3 = 12$
M4	$4 \times 3 = 12$
M5	$4 \times 3 = 12$
M6	$2 \times 3 = 6$
M7	$2 \times 3 = 6$
M8	$2 \times 3 = 6$
M9	$2 \times 3 = 6$
M10	$2 \times 3 = 6$
M11	4
M12	4
M13	4
M14	4
M15	6
M16	6
M17	6
M18	2
M19	2
M20	2
M21	2
M22	3
M23	3
M24	3

FA3:

Index of MOS	size
M1	$4 \times 4 = 16$
M2	$4 \times 4 = 16$
M3	$4 \times 4 = 16$
M4	$4 \times 4 = 16$
M5	$4 \times 4 = 16$
M6	$2 \times 4 = 8$
M7	$2 \times 4 = 8$
M8	$2 \times 4 = 8$
M9	$2 \times 4 = 8$
M10	$2 \times 4 = 8$
M11	4
M12	4
M13	4
M14	4
M15	6
M16	6
M17	6
M18	2
M19	2
M20	2
M21	2
M22	3
M23	3
M24	3

- (2) Based on the design of (1), run SPICE to find the propagation delay (As shown in Fig. 2, with pattern from IA [3:0] = 4'b1111, IB[3:0] = 4'b0000, IC_{in} = 1'b1 to IA[3:0] = 4'b1111, IB[3:0] = 4'b0000, IC_{in} = 1'b0). Determine the maximum propagation delay of the Ripple Carry Adder (exclude the load inverters). (20%)


Here's the waveform of C_{in} and S3:

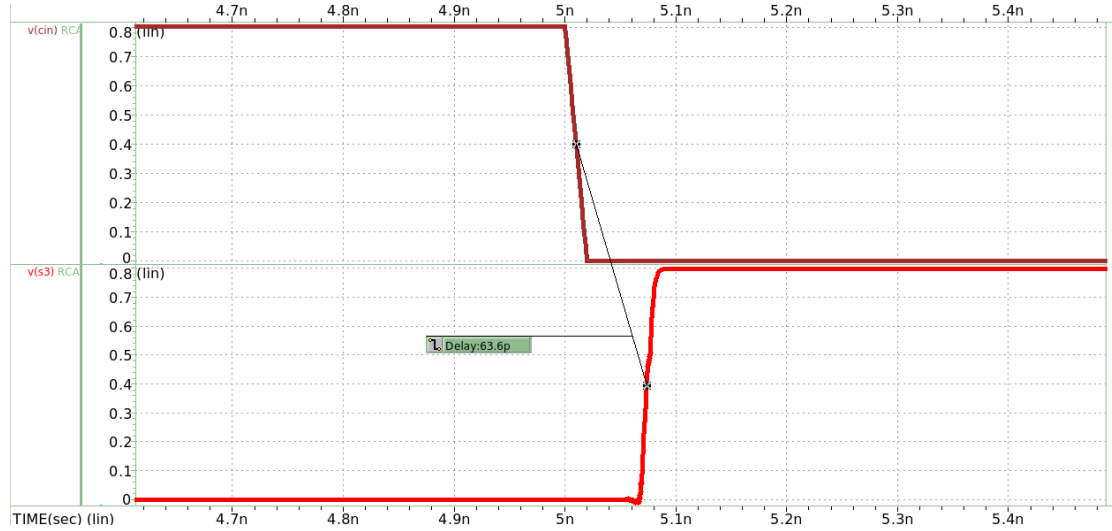

Therefore, the maximum propagation delay = 63.6ps.

- (3) Run SPICE of the ripple carry adder with each output load equals to 4 unit size inverter. Determine the average, peak, and leakage power dissipation and energy per bit, respectively when simulating at the working frequency in (2). (20%)

(a) Here's my pattern of input:

 


Note that the period of single pattern is 63.6ps.

Here's the simulation result of average power and peak power:

```
***** transient analysis tnom= 25.000 temp= 25.000 *****
avgpwr= 115.8002u from= 0. to= 1.3576n
peakpwr= 445.6248u at= 687.3335p
from= 0. to= 1.3576n
```

Therefore, average power = 115.8002uW and peak power = 445.6248uW.

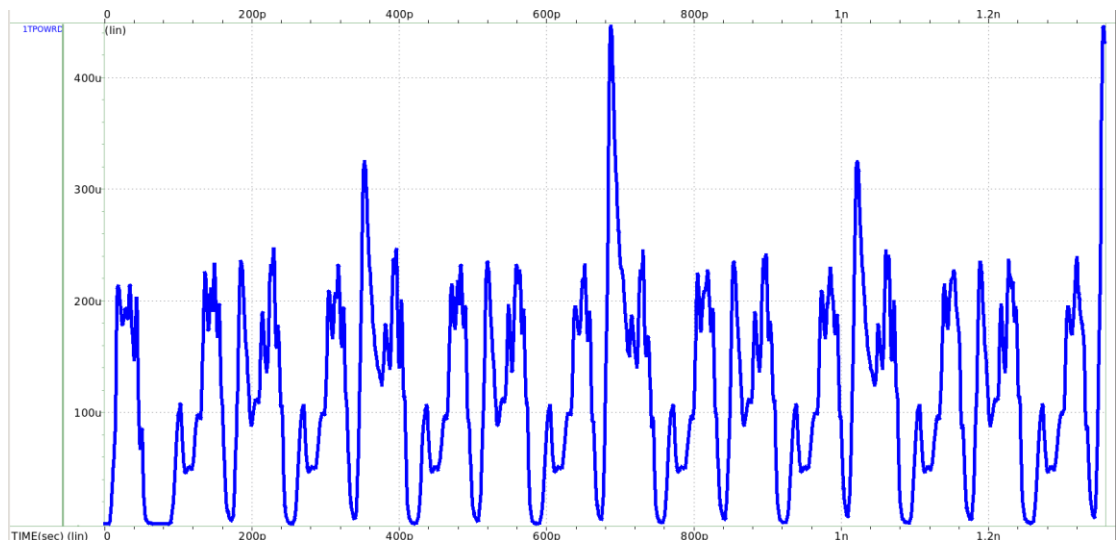(b) Here's the waveform of average power and peak power:



(c) Here's my code measuring leakage power:

```
.trans 1ps 16ns
V0 A0 gnd! 0v
V1 A1 gnd! 0v
V2 A2 gnd! 0v
V3 A3 gnd! 0v
V4 B0 gnd! xvdd
V5 B1 gnd! xvdd
V6 B2 gnd! xvdd
V7 B3 gnd! xvdd
V8 Cin gnd! 0v


.meas tran LeakagePower AVG power from = 0ns to = 16ns
```

(d) Here's the simulation result of leakage power:

```
***** transient analysis tnom= 25.000 temp= 25.000 *****
leakagepower= 4.2875n from= 0. to= 16.0000n
```

Therefore, leakage power = 4.2875nW

 (e) Here's the waveform of the leakage power:



(f) Energy/bit:

$$\text{Energy/bit} = (\text{avg_pwr} * \text{sim_time}) / \text{bit} = (115.8002\text{uW} * 1.3576\text{ns}) / 9 = 17.4678\text{fJ}$$


(g) Average power, peak power, leakage power, and energy/bit in table form:

Average power	115.8002uW
Peak power	445.6248uW
Leakage power	4.2875nW
Energy/bit	17.4678fJ

(4) Add pipelining stages as shown in Fig. 4 into the 4-bit ripple carry adder, with the D register given in Fig. 3. Run SPICE to find the propagation delay time (with pattern from IA [3:0] = 4'b0000, IB[3:0] = 4'b1111, IC_{in} = 1'b0 to IA[3:0] = 4'b0000, IB[3:0] = 4'b1111, IC_{in} = 1'b1) between pipelining stages to determine the maximum working frequency of the clock.

(a) Critical path is clk -> cin_dff -> s3.

 
(b) Here's the waveform including clk, cin, cin_dff, s3 and s3_dff:



Therefore, the max propagation delay = 64.4ps

 (c) 因為 propagation delay = 64.4ps, 所以 clk period 至少要大於 64.4 ps。在我反覆測試了幾次後，最終測出了 clk period 是 74ps 時 RCA 的功能會正確。

下圖是 clk period = 74ps 時的波型圖，可以看到 RCA 的功能是正確的。



(d) Maximum working frequency of the clock:

$$f = \frac{1}{T} = \frac{1}{74\text{ps}} = 13.513\text{GHz}$$

Therefore, the maximum working frequency of the clock = 13.513GHz